

# Task 1

NOT gates with BJT transistors (NPN)

a)RTL

\*foto del circuito\*

b) TTL

\*foto del circuito\*

## MEASSURES

Where  $V_{IH}$ : minimum HIGH input voltage,  $V_{IL}$ : maximum LOW input voltage,  $V_{OH}$ : minimum HIGH output voltage,  $V_{OL}$ : maximum LOW output voltage.

To measure these values we use the ramp waveform and the oscilloscope in xy mode so we can see something like this: \*fotis modo xy con puntos marcados\* Where the values we are looking for are found when the derivative is -1.

Noise margin :It allows one to estimate the allowable noise voltage on the input of a gate so that the output will not be affected. Noise margin is specified in terms of two parameters - the low noise margin NL, and the high noise margin NH . NL is defined as the difference in magnitude between the maximum LOW input voltage and the maximum LOW output voltage of the gate. That is,  $NL = -V_{IL} - V_{OL}$ . Similarly, the value of NH is the difference in magnitude between the minimum HIGH output voltage of and the minimum HIGH input voltage recognizable by the gate. That is,  $NH = -V_{OH} - V_{IH}$ .

The propagation delay is the difference in time (calculated at 50

Rise time is the time, during transition, when output switches from 10% Fall time is the time when output switches from 90%