

## Task 6

In this section, a D Flip-Flop and a SR Latch are implemented, based on logic gates.

### SR Latch

For the SR Latch, it is implemented using NOR gates of 74HC02 integrated circuit. The resulting schematic is shown below.

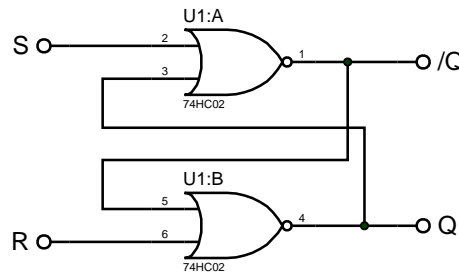


Figure 1: SR Latch circuit - Made in Proteus 7.8

PARAMETROS IMPORTANTES: PROPAGACION DE SET O RESET A LAS SALIDAS. MEDIR. COMPARAR CON UNO COMERCIAL CUALQUIERA

PARAMETER	FROM	TO	VALUE
$t_{pd}$	Circuit	S	Q
	74HC279	S	Q
$t_{pd}$	Circuit	R	Q
	74HC279	R	Q

Table 1: Measured values

### D Flip-Flop

For the D flip-flop, it is implemented using the SR Latch designed before, adding the remaining parts as shown below.

 


Figure 2: D Flip-Flop circuit - Made in Proteus 7.8

PARAMETROS IMPORTANTES: PROPAGACION DEL D A LA SALIDA LUEGO DEL CLK, TANTO PARA 0 COMO PARA 1. MEDIR. COMPARAR CON UNO COMERCIAL CUALQUIERA. The designed circuit will be compared with the 74HC74 D Flip-Flop, using the datasheet of Texas Instruments.

PARAMETER	FROM	TO	VALUE
$t_{pd}$	Circuit	CLK	Q or /Q
	74HC74	CLK	Q or /Q
$t_t$	Circuit		Q or /Q
	74HC74		Q or /Q

Table 2: Measured values